

Digital Techniques Practical Oral Question Bank

Unit No 1,2,3,4,5

Two Marks Questions

1. Define encoder, write the IC number of IC used as decimal to BCD encoder.
2. State the necessity of multiplexer.
3. Compare between synchronous and asynchronous counter (any two points).
4. Define shift register and list its types.
5. List triggering methods used for triggering flip flops.
6. Write truth table of D type flip-flop.
7. Draw logic diagram of T flip-flop and give its truth table.
8. Define modulus of a counter. Write the numbers of flip flops required for Mod-6 counter.
9. State function of preset and clear in flip flop.
10. Draw symbol and write truth table of D and T Flip Flop.
11. Write down number of flip flops are required to count 16 clock pulses.
12. State two specification of DAC
13. List any two specifications of IC-DAC 0808.
14. Define Resolution and conversion time associated with ADC.
15. List the types of DAC
16. List the types of ADC
17. List the types of Flipflop
18. Write truth table for SR FF
19. Write truth table for JK FF
20. Write truth table for D FF
21. Write truth table for T FF
22. Give the name of Universal gate? Why?
23. Draw symbol, truth table & Boolean equation for OR gate
24. Draw symbol, truth table & Boolean equation for NOT gate
25. Draw symbol, truth table & Boolean equation for AND gate
26. Draw symbol, truth table & Boolean equation for Ex-OR gate
27. Draw symbol, truth table & Boolean equation for Ex-NOR gate
28. Define min term & max term

29. State Demorgans Theorem
30. Define Fan in , fan out, propagation delay, power dissipation, figure of merit
31. List types of MUX
32. List types of DEMUX
33. List types of 7 segment display
34. Find 1's complement of 101011
35. Find 2's complement of 1011101
36. Give example of SOP & POS equation
37. List types of logic families
38. In which type both AND array & OR array is programmable? PAL or PLA
39. $(125)_{10} = (?)_2$
40. $(1011)_2 = (?)_{10}$
41. $(237)_8 = (?)_2$
42. $(101101111)_2 = (?)_8$
43. $(AD9)_{16} = (?)_{10}$
44. $(389)_{10} = (?)_{16}$
45. $(1011)_2 = (?)_{\text{gray}}$
46. $(10111)_{\text{gray}} = (?)_2$
47. $(76)_{10} = (?)_{\text{BCD}}$
48. List types of PLD
49. Ripple counter is also called as? Asynchronous or Synchronous
50. Write AND Law
51. Write OR law